



①  
TD+

↳ la fonction de transfert  $\frac{V_c}{V_s} = \frac{V_c/V_r}{E}$

Ans:

$$V_c = V_L + V_R = L \frac{di_r}{dt} + R i_r \quad (1)$$

$$I = I_R + I_C \quad (2)$$

$$V_R = V_C \quad (3)$$

$$(1) \Rightarrow V_c = L \frac{d}{dt} (I_R + I_C) + R i_r$$

$$V_c = L \frac{dI_R}{dt} + L \frac{dI_C}{dt} + R i_r$$

$$3) \Rightarrow R i_r = \frac{1}{C} \int i_c \cdot dt \Rightarrow$$

$$\frac{dI_C}{dt} = RC \frac{di_r}{dt} \Rightarrow (4) \quad (4)$$

$$V_c = L \frac{dI_R}{dt} + L \left( RC \frac{di_r}{dt} \right) + R i_r$$

$$V_c = LRC \frac{d^2 i_r}{dt^2} + L \frac{di_r}{dt} + R i_r$$

Laplace

$$V_c(p) = LRC i_{rp} + L i_{rp} + R i_r(p) \quad (5)$$

$$V_s(p) = R i_r(p) \rightarrow (6)$$

$$\frac{V_s(p)}{V_c(p)} = \frac{R i_r(p)}{LRC i_{rp} + L i_{rp} + R i_r(p)}$$

$$\frac{V_s(p)}{V_c(p)} = \frac{TRR}{LRCp^2 + Lp + R}$$

$$AN: (R=2, L=C=1, V=1)$$

$$\frac{V_s(p)}{V_c(p)} = \frac{2}{2p^2 + p + 2}$$

2) l'équation d'état de sys

$$(1) \Rightarrow$$

$$\frac{dV_c}{dt} = -\frac{R}{L} i_r + \frac{V_c}{L} \quad (4) \quad (4)$$

$$\text{Ans: } (4) \Rightarrow$$

$$\frac{di_r}{dt} = \frac{1}{RC} i_c \rightarrow (4)$$

$$(3) \Rightarrow$$

$$\textcircled{3} \Rightarrow v_e = L \frac{d}{dt} (i_r + i_c) + R i_r$$

$$v_e = L \frac{di_r}{dt} + L \frac{di_c}{dt} + R i_r$$

mais  $\textcircled{4} \Rightarrow \frac{di_r}{dt} = \frac{1}{R_c} i_c$  donc

$$v_e = \frac{L}{R_c} \ddot{i}_c + L \frac{di_c}{dt} + R i_r \Rightarrow$$

$$\frac{di_c}{dt} = \frac{v_e}{L} - \frac{1}{R_c} i_c - \frac{R}{L} i_r \quad \rightarrow$$

$$\begin{cases} \frac{di_r}{dt} = -\frac{R}{L} i_r + \frac{1}{L} v_e \\ \frac{di_r}{dt} = \frac{1}{R_c} i_c \end{cases} \quad \begin{matrix} \text{AN}^{\circ} X = \begin{pmatrix} 0 & -2 & 0 \\ 0 & 0 & 1 \\ 0 & -2 & -\frac{1}{2} \end{pmatrix} \\ B \begin{pmatrix} 1 \\ 0 \\ 1 \end{pmatrix} \end{matrix} \quad \text{just}$$

$$\frac{di_c}{dt} = -\frac{R}{L} i_r - \frac{1}{R_c} i_c + \frac{v_e}{L}$$

En pos:  $i(eL) = x_i \Rightarrow \dot{x}_1 = \frac{di_r}{dt}$   
 $i_r = x_2 \Rightarrow \dot{x}_2 = \frac{di_r}{dt}$   
 $i_c = x_3 \Rightarrow \dot{x}_3 = \frac{di_c}{dt}$

$$\begin{pmatrix} \dot{x}_1 \\ \dot{x}_2 \\ \dot{x}_3 \end{pmatrix} = \begin{pmatrix} 0 & -\frac{R}{L} & 0 \\ 0 & 0 & \frac{1}{R_c} \\ 0 & -\frac{R}{L} & -\frac{1}{R_c} \end{pmatrix} \begin{pmatrix} x_1 \\ x_2 \\ x_3 \end{pmatrix} + \begin{pmatrix} \frac{1}{L} \\ 0 \\ \frac{1}{L} \end{pmatrix} v_e$$